

**ELECENG 3EJ4:Electronic Devices and Circuits II**



**Lab 3: Multistage Amplifiers**

**Clara Dawang (dawangc, 400329049)**

**03Nov2024**

## Questions for Part 1

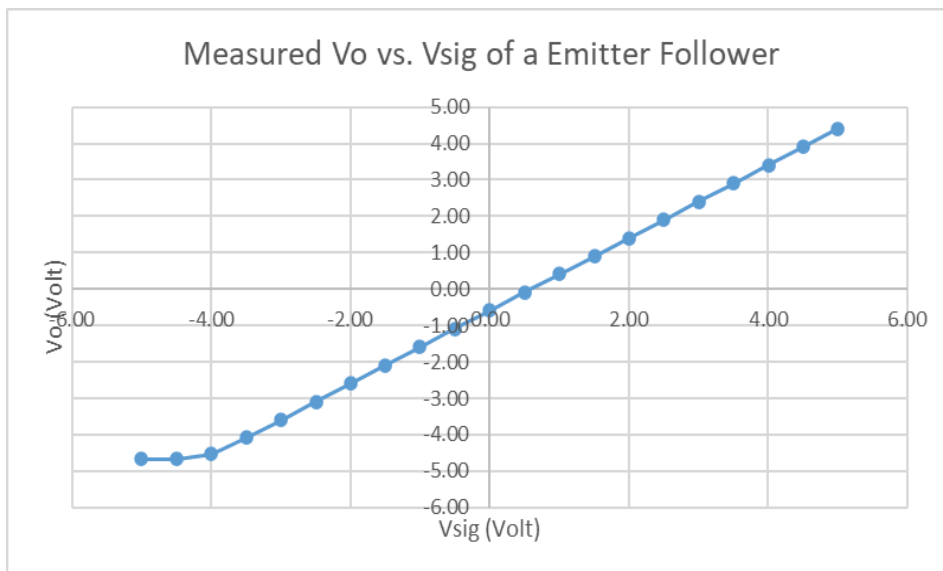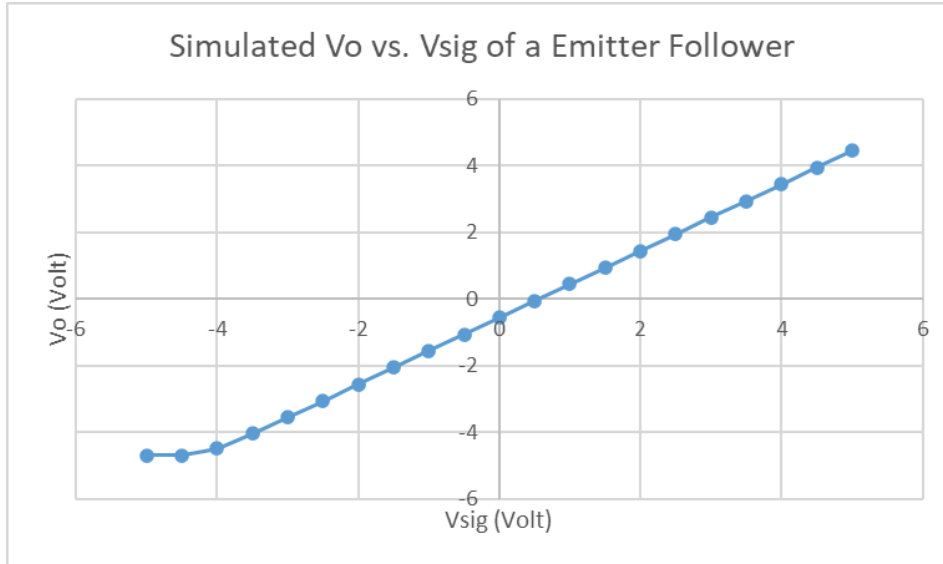1. a) The graphs for the simulated and measured  $V_o$  vs  $V_{sig}$  characteristics are shown in the graphs below.



The graphs demonstrate a linear relationship between  $V_o$  and  $V_{sig}$ , trending upwards. Both graphs portray the same overall shape and range of both  $V_o$  and  $V_{sig}$  values.

b) To ensure the circuit works as a common-collector (CC) amplifier, the DC input range for  $V_{sig}$  is between -4.5V and 5V. Based on collected data, the corresponding output  $V_o$  range is between -4.6 and 4.5V.

c) When  $V_{sig} = 0.5V$ ,  $V_o \approx 0$ .

2. In step 1.3, the simulated intrinsic voltage gain is 0.00dB with a phase of  $-8.47\text{E-}5^\circ$ . In step 1.8, the measured intrinsic voltage gain is 0.8dB with a phase of  $-8.47\text{E-}5^\circ$ .

### Questions for Part 2

Q3. a) Based on the textbook section, if Q2 is matched to Q1 (when the EBJ area of Q2 is equal to the EBJ area of Q1), then  $I_o = I_{REF}$ .


b) Based on the simulation data, when  $I_{REF} = 0.0001\text{A}$ ,  $I_o = 0.000104\text{A}$ . When  $I_{REF} = 0.001\text{A}$ ,  $I_o = 0.000975\text{A}$ .

3) Theoretically,  $I_{REF}$  and  $I_o$  should be equal values. However, when simulated, there was a small discrepancy between  $I_o$  and  $I_{REF}$  in each case. When  $I_{REF}$  was 0.1mA,  $I_o$  was different by 0.04A. When  $I_{REF}$  was 1mA,  $I_o$  was different by 0.025A. Therefore, the simulated values were very close to the theoretical values, and the differences can be attributed to simulation parameters and circumstances.

Q4. a) Based on the simulation data obtained in step 2.5, the output impedance  $h_{11} = R_{in} = 389.12\ \Omega$ . The current gain  $h_{21} = A_i = 1.04\ \text{A/A}$ .

b) Based on the simulation data obtained in step 2.6, the output impedance  $R_o = 1.58\text{E}6\ \Omega$ .

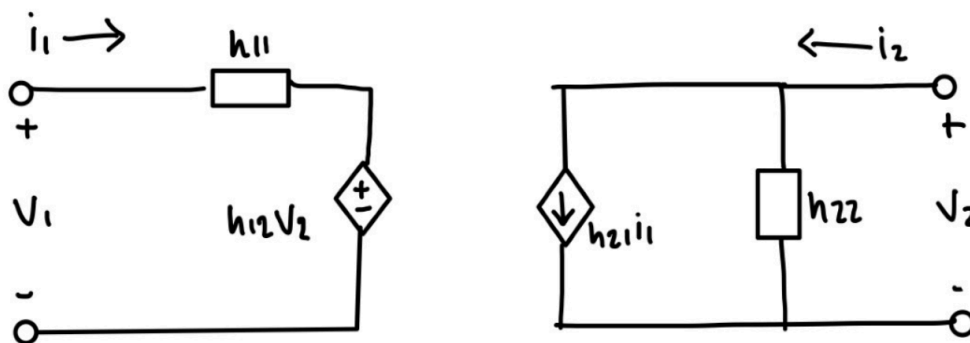c) the linear two-port network for the current mirror using h-parameters is shown below:



With h parameters from the excel sheet:

$h_{11} = R_{in} = 389.12\ \Omega$

$h_{12} = 7.05\text{E-}07\ \text{V/V}$  (at 100Hz) to  $h_{12} = 1.41\text{E-}06\ \text{V/V}$  (at 200Hz)

$h_{21} = 1.04\ \text{A/A}$

$h_{22} = 1.01\text{E-}04\ \text{S}$

### Questions for Part 3

Q5. a) Based on the simulation data obtained in step 3.2, the voltage gain  $A_d = 70.07\text{dB}$ .

b) In step 3.6, there was a mismatch of  $0.00725\text{V}$  observed. This value was used as the offset voltage applied at  $V_2$ .

c) The measured gain in step 3.8 was observed as  $58.9\text{dB}$ . This value is smaller than the gain recorded in step 3.2, which was  $70.07\text{dB}$ . This discrepancy can be attributed to the noise from the AD2, and the fact that the exact placement of the Y cursors to perform the measurements are subjective based on the user.

Q6. At low frequencies, the  $V_o$  amplitude is  $6.3786\text{V}$ .  $70.7\%$  of this low frequency value is  $(0.707)(6.3786\text{V}) = 4.5096\text{V}$ . In sheet 3.2, this magnitude corresponds to the frequency  $11207.40201\text{Hz}$ .

Q7. In Q8 of Lab 2, the upper 3-dB frequency was determined to be  $8145\text{kHz}$ . This is much greater than the  $11\text{kHz}$  found in Q6 of lab 3. The differential amplifier with a current mirror load has this smaller 3dB frequency because of increased effective capacitance at the amplifier input. This is called the Miller effect, which reduces the direct gain of an amplifier at high frequencies.

Q8. With the resistive load in Lab 2, the GBW was  $7.95\text{E}+07\text{Hz}$ . With the current mirror load in Lab 3, GBW was  $3.57\text{E}+07\text{Hz}$ .