

3EJ4: Electronic Devices and Circuits II

Lab 1: Device Characterization and Biasing Circuits

Clara Dawang (dawangc, 400329049)

22Sep2024

C. Questions for part 1

Q1. The following questions were answered from the simulated circuit in Part 1, shown below. The simulation run data was extracted and inserted in sheet “Steps 1.2-1.4” of the attached Excel file.

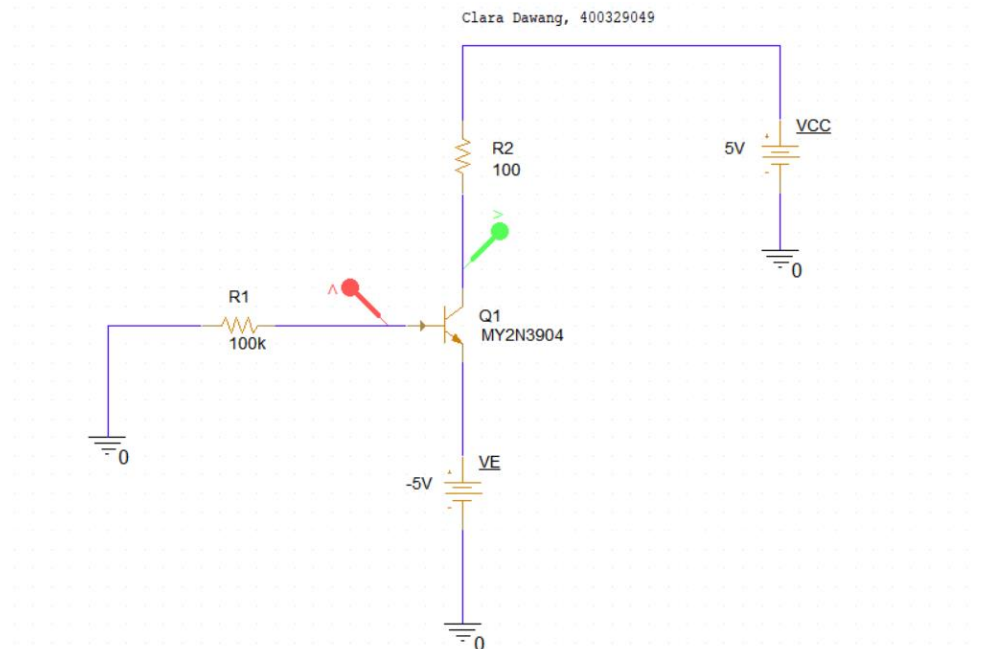


Figure 1 – Part 1 PSpice Schematic

If the device is biased to conduct a collector current $I_C \approx 1.00$ mA at the lowest V_{CE} value:

1. $V_{BEon} = 0.621$ V and the base current $I_B = 8.79$ μ A
2. $\beta = I_C/I_B = 117$
3. $|V_A| = 1000$ V
4. $r_o = 976$ k Ω
5. $g_m = 41$ ms
6. $r_\pi = 2.845$ k Ω

Q2. The following questions were answered from the measured data in step 1.8, using the same bias condition found in Q1 above.

1. $I_C = 2.16$ mA
2. $V_{BEon} = 0.6604$ V and the base current $I_B = 8.40$ μ A
3. $\beta = I_C/I_B = 257$
4. $|V_A| = 210$ V
5. $r_o = 97.4$ k Ω
6. $g_m = 86.2$ ms
7. $r_\pi = 2.978$ k Ω

C. Questions for part 2

Q3. The following questions were answered from the simulated circuit in Part 2, shown below. The simulation run data was extracted and inserted in sheet “Steps 2.2-2.4” of the attached Excel file.

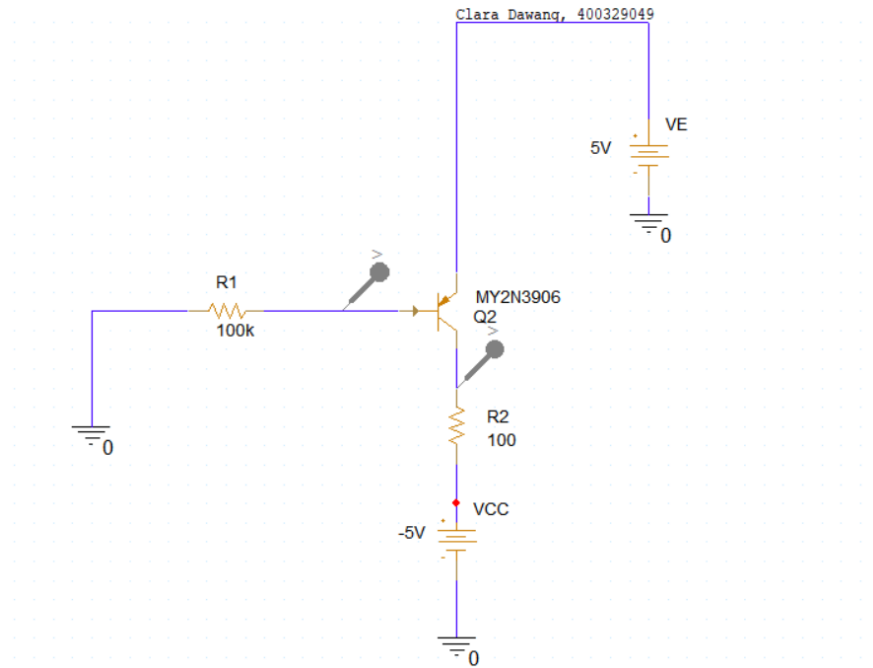


Figure 2 - Part 2 PSpice Schematic


If the device is biased to conduct a collector current $I_C \approx 1.00$ mA at the lowest V_{CE} value:

1. $V_{BEon} = 0.660$ V and the base current $I_B = 8.40$ μ A
2. $\beta = I_C/I_B = 123$
3. $|V_A| = 143$ V
4. $r_o = 139$ k Ω
5. $g_m = 41.2$ ms
6. $r_\pi = 2.976$ k Ω

Q4. The following questions were answered from the measured data in step 1.8, using the same bias condition found in Q3 above.

1. $I_C = 1.92$ mA
2. $V_{BEon} = 0.658$ V and the base current $I_B = 8.42$ μ A
3. $\beta = I_C/I_B = 228$
4. $|V_A| = 26$ V
5. $r_o = 13.5$ k Ω
6. $g_m = 76.8$ ms
7. $r_\pi = 2.969$ k Ω

Q5.

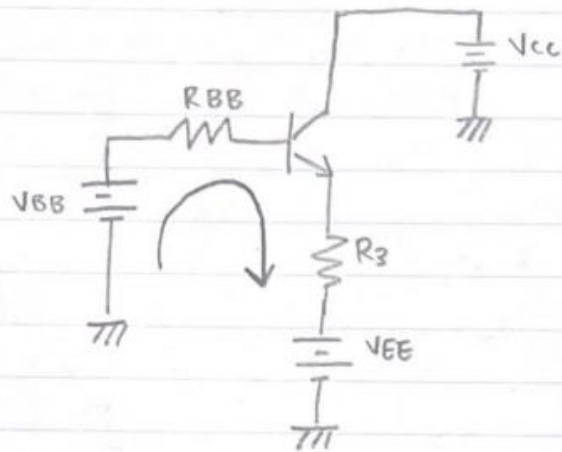

Clara Dawang
400329049

$$I_B = I_E - I_C$$

$$I_C = \beta I_B$$

$$I_B + \beta I_B = I_E$$

$$I_B(1 + \beta) = I_E$$

$$0 + V_{BB} - I_B R_{BB} - V_{BE} - I_E R_3 - V_{EE} = 0$$

$$V_{BB} - I_B R_{BB} - V_{BE} - I_B(1 + \beta) R_3 - V_{EE} = 0$$

$$V_{BB} - V_{BE} - V_{EE} = I_B R_{BB} + I_B(1 + \beta) R_3$$

$$V_{BB} - V_{BE} - V_{EE} = I_B(R_{BB} + (1 + \beta) R_3)$$

$$I_B = \frac{V_{BB} - V_{BE} - V_{EE}}{R_{BB} + R_3(1 + \beta)}$$

Q6.

Difference between equation (3) and equation from Q.5 is the second denominator term:

$$\text{equation (3): } I_B = \frac{V_{BB} - (V_E + V_{BE_{on}})}{R_{BB}}$$

$$\text{question 5: } I_B = \frac{V_{BB} - V_E - V_{BE_{on}}}{R_{BB} + R_3(1 + \beta)}$$

Equation (3) with ΔV_{EE}

$$I_B = \frac{R_2}{R_1 + R_2} - \frac{V_{EE}}{R_{BB}} - \frac{V_{BE_{on}}}{R_{BB}}$$

$$I_{B_{end}} = \frac{R_2}{R_1 + R_2} - \frac{(V_{EE} + \Delta V_{EE})}{R_{BB}} - \frac{V_{BE_{on}}}{R_{BB}}$$

$$\Delta I_B = \left(\frac{R_2}{R_1 + R_2} - \frac{V_{EE}}{R_{BB}} - \frac{V_{BE_{on}}}{R_{BB}} \right) - \left(\frac{R_2}{R_1 + R_2} - \frac{(V_{EE} + \Delta V_{EE})}{R_{BB}} - \frac{V_{BE_{on}}}{R_{BB}} \right)$$

$$\Delta I_B = \left(\frac{R_2}{R_1 + R_2} \right) \left(-\frac{\Delta V_{EE}}{R_{BB}} \right)$$

Question 5 with ΔV_{EE} :

$$I_B = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{-V_{EE}}{R_{BB} + R_3(1+\beta)} \right) - \frac{V_{BE_{ON}}}{R_{BB} + R_3(1+\beta)}$$

$$I_{B_{end}} = \frac{R_2}{R_1 + R_2} \left(\frac{-(V_{EE} + \Delta V_{EE})}{R_{BB} + R_3(1+\beta)} \right) - \frac{V_{BE_{ON}}}{R_{BB} + R_3(1+\beta)}$$

$$\Delta I_B = \left(\left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{-(V_{EE} + \Delta V_{EE})}{R_{BB} + R_3(1+\beta)} \right) - \frac{V_{BE_{ON}}}{R_{BB} + R_3(1+\beta)} \right) - \left(\left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{-V_{EE}}{R_{BB} + R_3(1+\beta)} \right) - \frac{V_{BE_{ON}}}{R_{BB} + R_3(1+\beta)} \right)$$

$$\Delta I_B = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{-\Delta V_{EE}}{R_{BB} + R_3(1+\beta)} \right)$$

Final Comparison with ΔV_{EE}

$$\text{equation (3): } \Delta I_B = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{-\Delta V_{EE}}{R_{BB}} \right)$$

$$\text{question 5: } \Delta I_B = \left(\frac{R_2}{R_1 + R_2} \right) \left(\frac{-\Delta V_{EE}}{R_{BB} + R_3(1+\beta)} \right)$$

When there is change ΔV_{EE} applied, the R_3 term is present in the denominator of the question 5 equation. As ΔV_{EE} is divided by R_3 in this term, the emitter resistor reduces the change in the base current.

Q7.

When $R_3 \neq 0$:

$$\begin{aligned} V_{O, \min} &= V_{EE} + I_E R_3 + 0.3 \text{ V} \\ &= V_{EE} + I_O R_3 + 0.3 \text{ V} \\ &= V_{EE} + 1 \text{ mA}(R_3) + 0.3 \text{ V} \end{aligned}$$

Q8.

$$V_{0, \min} = V_{EE} + I_{mA} R_3 + 0.3$$

$$-1.5V = -5V + R_3 + 0.3$$

$$R_3 = 3.2 \text{ k}\Omega$$

$$\text{at node } V_{BB}: V_{BB} - I_B R_{BB} - V_B = 0$$

$$V_B - V_{BE} - I_E R_3 - V_{EE} = 0$$

$$V_B = 0.621 + \frac{118}{117} (3.2) - 5$$

$$V_B = -1.15165$$

Substitute V_B and R_{BB} using lab manual equation ②

$$V_{BB} = I_B \left(\frac{R_1 R_2}{R_1 + R_2} \right) - 1.15165$$

using lab manual equation ①

$$V_{BB} = V_{EE} \left(\frac{R_1}{R_1 + R_2} \right)$$

$$-5 \left(\frac{R_1}{R_1 + 100K} \right) = \frac{1}{117} \left(\frac{100K R_1}{100K + R_1} \right) - 1.15165$$

$$\frac{-5R_1 - 0.8547R_1}{100K + R_1} = -1.15165$$

$$-5.8547R_1 = -1.15165(100K + R_1)$$

$$-5.8547R_1 = -115.165K - 1.15165R_1$$

$$-5.8547R_1 + 1.15165R_1 = -115.165K$$

$$-4.6982R_1 = -115.165K$$

$$R_1 = 24.51258 \text{ k}\Omega$$

To verify the above results, the following circuit was constructed in PSpice and used to sweep V_{CC} from -5V to 5V.

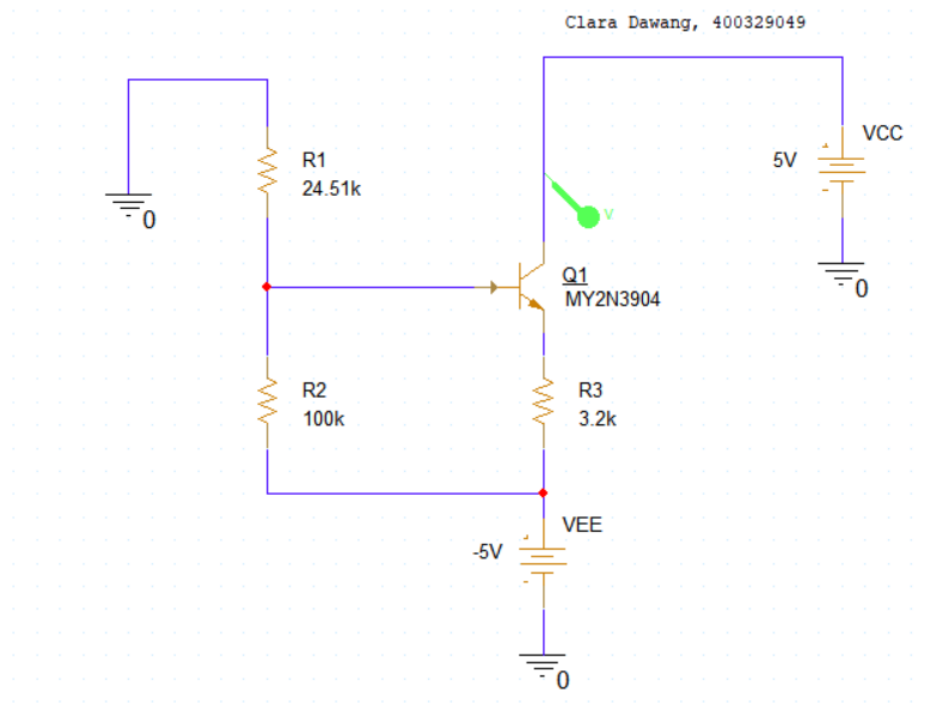


Figure 3 – Question 8 PSpice Schematic

The following waveform was obtained, with the voltage V_{CC} plotted in green and the output current I_o (I_C) plotted in red.

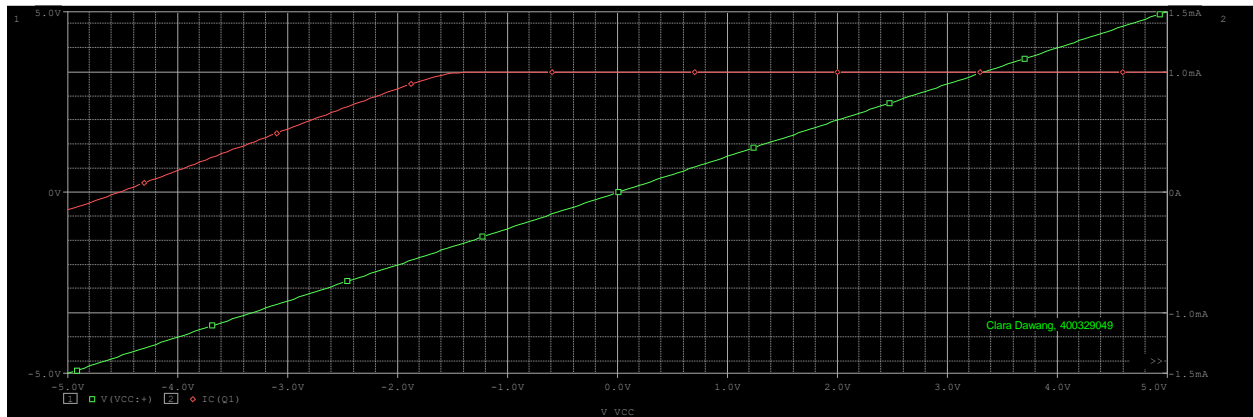


Figure 4 - Question 8 waveform of I_o vs. V_{cc}

Q9. The circuit in Figure 3 shows a DC sweep of V_{CC} to measure V_E (green) and I_C (red), shown in the waveform below.

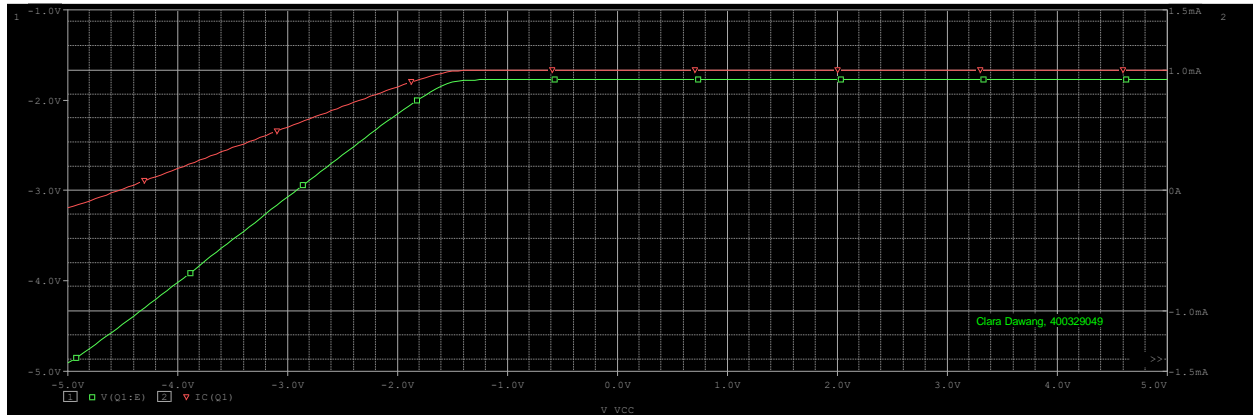


Figure 5 - Question 9 waveform of V_E and I_C

The active region is shown by the flat collector current I_C . When the horizontal trend begins, $V_C \approx -1.2V$. At this point, the V_E value is extrapolated to be $-1.7744V$. To find V_{CE} :

$$V_{CE} = V_C - V_E$$

$$V_{CE} = |-1.2V| - |-1.7744V|$$

$$V_{CE} = |-0.5744V|$$

$$|0.5744V| \geq 0.3V$$

Therefore, when the condition $|V_{CE}| \geq 0.3V$ is met and Q_1 is in active region, the $|V_{CE}|$ required is approximately $|0.5744V|$.